

## Frequency Response Blitz

For each BJT amplifier given, find the total frequency response.  
Assume the following BJT parameters:

Let  $c_{\pi} = 5\text{pF}$ ,  $c_{\mu} = 2\text{pF}$ ,  $\beta = 100$ ,  $V_A = 150$

